



STANFORD

Supplementary Lecture 4A

Transmission-Line Channels

JOHN M. CIOFFI

Hitachi Professor Emeritus (recalled) of Engineering

Instructor EE379A – Winter 2026

Announcements & Agenda

- Goals
 - Familiarize, or reacquaint, interested students/researchers to obtain an $H(f)$ for a transmission line
 - Permit construction of real or complex baseband-equivalent channels for analysis.

This is first of 3 short lectures online

S4A: Transmission Line



S4B: Waveguide

S4C: Wireless (with antennas)

- Topics
 - Filtered AWGN
 - 2-port network review & transmission line
 - Phases and delays
 - Cascades
 - Example use rlcg379.m




Finding $H(f)$

Section 1.3.8

Computation of $H(f)$

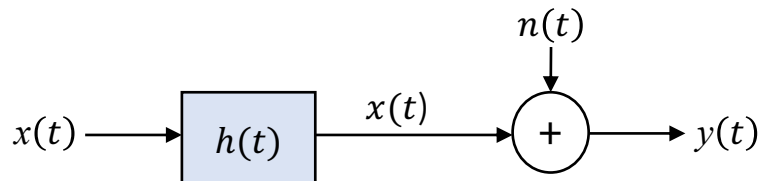
- **Channel filter** $h(t) \leftrightarrow H(f)$ from electromagnetic modelling.



- **Noise:** AWGN often specifies a PSD, like -174 dBm/Hz
 - This is room temperature noise $k \cdot T$ (Boltzman constant x Kelvin temperature).
 - Often ADC quantization and/or background noises lifts this to numbers like -150 dBm/Hz , or “noise figure” in dB increases this level
 - Unrelated radio noises can “color” the noise (must measure $S_{noise}(f)$) and then can model with noise-whitening receiver that changes $H(f) \leftrightarrow S_{noise}^{-1/2} \cdot H(f)$



Supplementary – 2-port Network

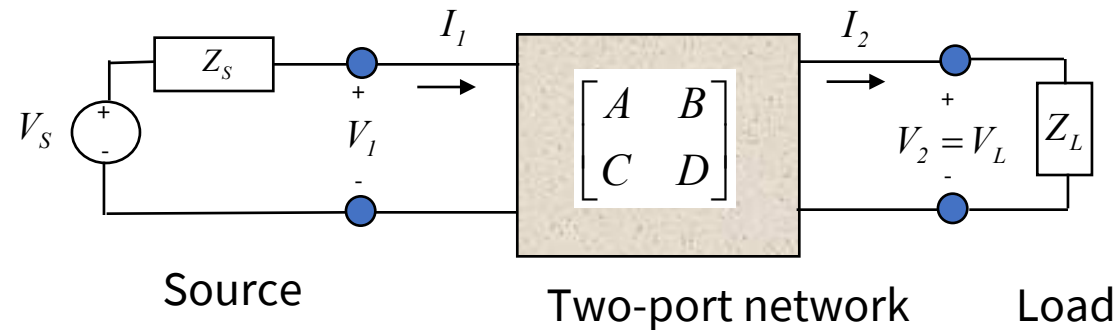

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \underbrace{\begin{bmatrix} A & B \\ C & D \end{bmatrix}}_{\Phi} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

- **Overall Transfer Function follows.**

➤ By cascading sections

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \left(\prod_{i=1}^{N-1} \Phi_i \right) \cdot \begin{bmatrix} V_N \\ I_N \end{bmatrix}$$


- **Overall Transfer Function is:** $\frac{V_L}{V_S} = \frac{Z_1}{Z_1 + Z_S} \cdot \frac{Z_L}{A \cdot Z_L + B}$ where $Z_1 = \frac{A \cdot Z_L + B}{C \cdot Z_L + D}$

Transfer function = “Insertion Loss” + 6db (IL = measure w & w/o 2-port present)



Supplementary – Transmission Line

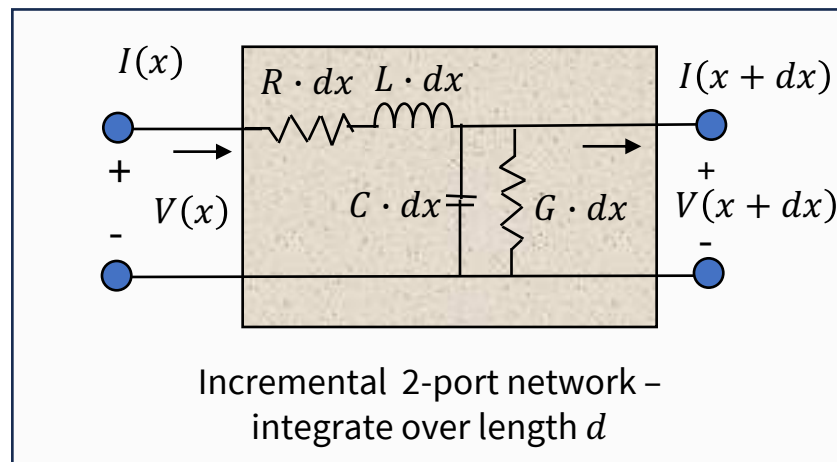- Cascade sections and integrate.
- Propagation constant is
 - $\gamma = \sqrt{(R + j\omega L) \cdot (G + j\omega C)}$
- Characteristic Impedance is
 - $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$
- RLCG 1.3.8 tables



$$\frac{V_L}{V_S} = \frac{Z_0 \cdot \operatorname{sech}(\gamma \cdot d)}{Z_0 \cdot \left[Z_0 / Z_L + \tanh(\gamma \cdot d) \right] + Z_0 \cdot \left[1 + Z_0 / Z_L \cdot \tanh(\gamma \cdot d) \right]}$$

Appendix E (when complete) provides more details. The length is d .



Velocity, Phase, and Delay

- $\cos(\omega \cdot t + \theta)$ = sinusoid propagating (whatever amplitude)
- **Phase delay** is $\tau_p = -\frac{\theta}{\omega}$; **phase velocity** is $v_p = -\frac{\omega}{\beta}$
- **Group delay** is $\tau_g = -\frac{d\theta}{d\omega}$; **group velocity** is $v_g = -\frac{d\omega}{d\beta}$
- Lossless (R=G=0), then $c_{tl} = \frac{1}{\sqrt{LC}} \leq c = 3 \times 10^8 \text{ m/s}$
 - $c_{tl} = \sqrt{v_p \cdot v_g}$





Average Group Delay & RMS Delay Spread

- **Average group delay** $\langle \tau_g \rangle = \frac{\int_0^\infty t \cdot |h(t)|^2 \cdot dt}{\int_0^\infty |h(t)|^2 \cdot dt}$
- **Average group delay** $\tau_{rms} = \frac{\int_0^\infty (t - \tau_g)^2 \cdot |h(t)|^2 \cdot dt}{\int_0^\infty |h(t)|^2 \cdot dt}$



Single Line or Sections

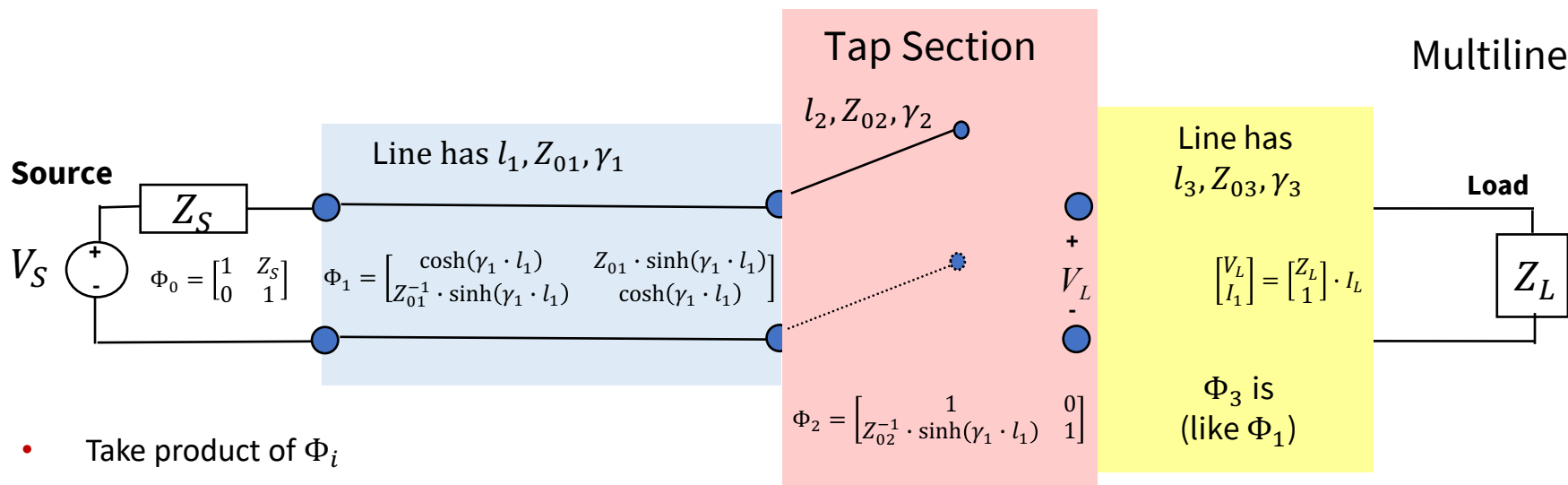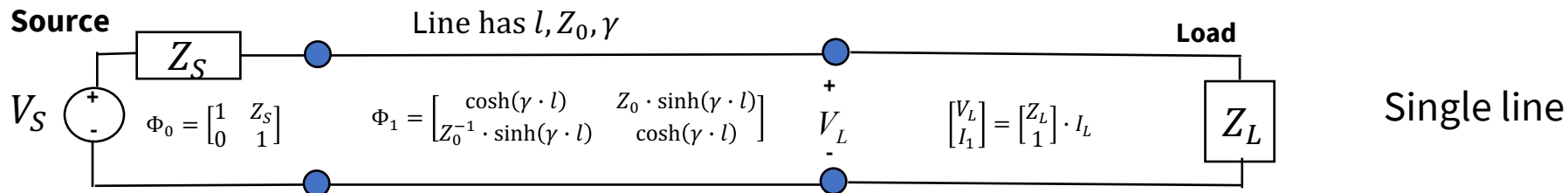

- Take product of Φ_i
 - Can add 2-port circuits like transformers
 - or “baluns” (impedance matching circuits between trans line and waveguide), etc




Example

- Matlab `rlcg379`.
 - Inputs $R, L, C, G, l, Z_s, Z_L, f$
 - Outputs $H, Z_{in}, ABCD$
 - Also plots magnitude and phase on $\log(f)$ scale

```
f = logspace(1, 8, 1000);  
R = 0.1 + 0.01 * sqrt(f); % Example: Resistance in ohms/m  
L = 1e-6 * ones(size(f)); % Example: Inductance in H/m  
C = 100e-12 * ones(size(f)); % Example: Capacitance in F/m  
G = 1e-9 * ones(size(f)); % Example: Conductance in S/m  
l = 10; % Length in meters  
Z_s = 50; % Source impedance in ohms  
Z_L = 100; % Load impedance in ohms  
H,Z_in,ABCD]=rlcg379(R,L,C,G,l,Z_s,Z_L,f);  
size(ABCD) % =      2      2    1000
```

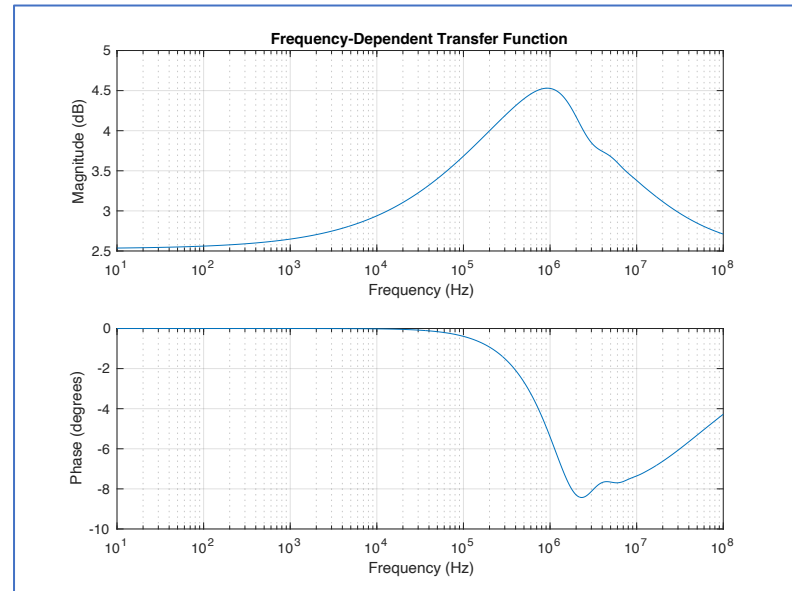- Insertion loss, divide by 2
 - If $Z_s \sim \text{matches } Z_{in}$





End Supplementary Lecture 4A